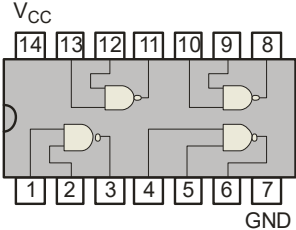



Summary

Fixed Function Logic


Some common gate configurations are shown.




'00

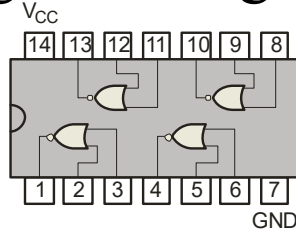


'02

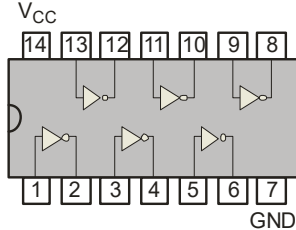


'04

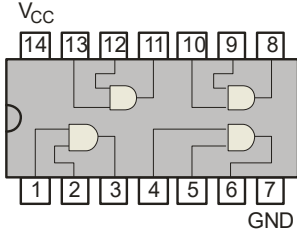


'08

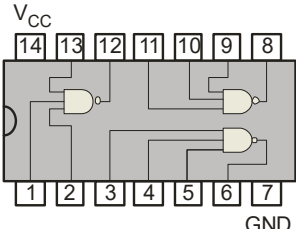


'10

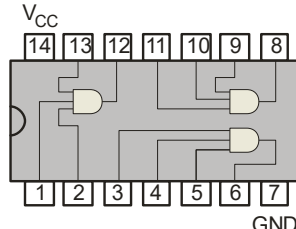


'11

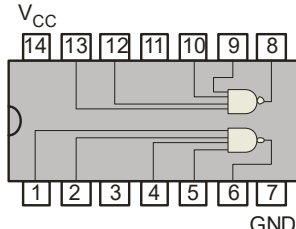


'20

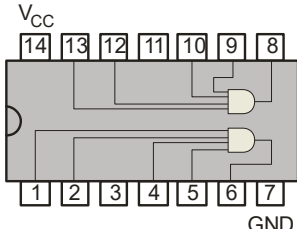


'21

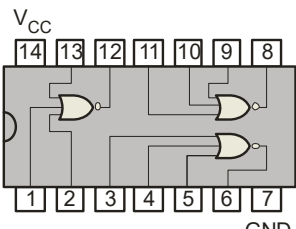


'27

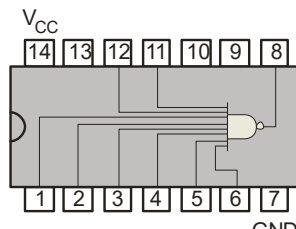

'30

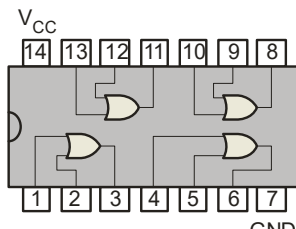

'32

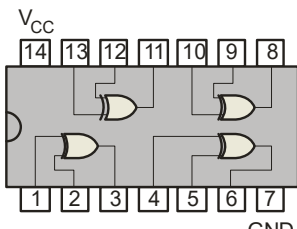

'86