


---

---

---

---

---

---

---

---

**Summary**

**Latches**

A **latch** is a temporary storage device that has two stable states (bistable). It is a basic form of memory.

The S-R (Set-Reset) latch is the most basic type. It can be constructed from NOR gates or NAND gates. With NOR gates, the latch responds to active-HIGH inputs; with NAND gates, it responds to active-LOW inputs.

The diagram shows a cross-coupled NOR gate configuration. The top NOR gate has inputs  $R$  and  $Q$ , and its output is  $\bar{Q}$ . The bottom NOR gate has inputs  $S$  and  $\bar{Q}$ , and its output is  $Q$ . The inputs  $R$  and  $S$  are labeled as active-HIGH.

NOR Active-HIGH Latch

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

**Summary**

**Latches**

The active-HIGH S-R latch is in a stable (latched) condition when both inputs are LOW.

Assume the latch is initially RESET ( $Q = 0$ ) and the inputs are at their inactive level (0). To SET the latch ( $Q = 1$ ), a momentary HIGH signal is applied to the  $S$  input while the  $R$  remains LOW.

The diagram shows the same cross-coupled NOR gate circuit as above. It includes timing signals: a blue pulse for the  $S$  input and a red pulse for the  $R$  input. The output  $Q$  is shown as a blue pulse that occurs when  $S$  is high and  $R$  is low. The output  $\bar{Q}$  is shown as a red pulse that occurs when  $R$  is high and  $S$  is low. The text 'Latch initially RESET' is placed near the  $Q$  output line.

To RESET the latch ( $Q = 0$ ), a momentary HIGH signal is applied to the  $R$  input while the  $S$  remains LOW.

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

**Summary**


**Latches**

The active-LOW  $\bar{S}$ - $\bar{R}$  latch is in a stable (latched) condition when both inputs are HIGH.

Assume the latch is initially RESET ( $Q = 0$ ) and the inputs are at their inactive level (1). To SET the latch ( $Q = 1$ ), a momentary LOW signal is applied to the  $\bar{S}$  input while the  $\bar{R}$  remains HIGH.

To RESET the latch a momentary LOW is applied to the  $\bar{R}$  input while  $\bar{S}$  is HIGH.

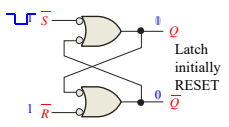Never apply an active set and reset at the same time (invalid).



Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

**Summary**



**Latches**

The active-LOW  $\bar{S}$ - $\bar{R}$  latch is available as the 74LS279A IC.

It features four internal latches with two having two  $\bar{S}$  inputs. To SET any of the latches, the  $\bar{S}$  line is pulsed low.

It is available in several packages.

$\bar{S}$ - $\bar{R}$  latches are frequently used for switch debounce circuits as shown:

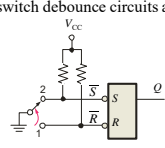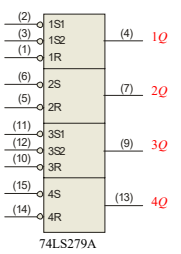Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

**Summary**



**Latches**

A gated latch is a variation on the basic latch.

The gated latch has an additional input, called enable ( $EN$ ) that must be HIGH in order for the latch to respond to the  $S$  and  $R$  inputs.

**Example** Show the  $Q$  output with relation to the input signals. Assume  $Q$  starts LOW.

**Solution** Keep in mind that  $S$  and  $R$  are only active when  $EN$  is HIGH.

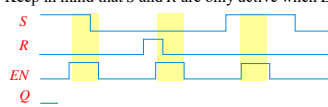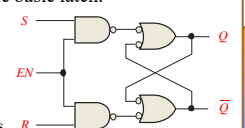Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

**Summary**

**Latches**

The *D* latch is an variation of the *S-R* latch but combines the *S* and *R* inputs into a single *D* input as shown:

A simple rule for the *D* latch is:  
*Q* follows *D* when the Enable is active.

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**Latches**

The truth table for the *D* latch summarizes its operation. If *EN* is LOW, then there is no change in the output and it is latched.

Inputs		Outputs		Comments
<i>D</i>	<i>EN</i>	<i>Q</i>	$\bar{Q}$	
0	1	0	1	RESET
1	1	1	0	SET
X	0	$Q_0$	$\bar{Q}_0$	No change

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**Latches**

**Example**

Determine the *Q* output for the *D* latch, given the inputs shown.

Notice that the Enable is not active during these times, so the output is latched.

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**Flip-flops**

A flip-flop differs from a latch in the manner it changes states. A flip-flop is a clocked device, in which only the clock edge determines when a new bit is entered.

The active edge can be positive or negative.

(a) Positive edge-triggered      (b) Negative edge-triggered

Floyd, Digital Fundamentals, 10<sup>th</sup> ed      © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**Flip-flops**

The truth table for a positive-edge triggered D flip-flop shows an up arrow to remind you that it is sensitive to its *D* input only on the rising edge of the clock; otherwise it is latched. The truth table for a negative-edge triggered D flip-flop is identical except for the direction of the arrow.

Inputs		Outputs		Comments
<i>D</i>	CLK	<i>Q</i>	$\bar{Q}$	
1	↑	1	0	SET
0	↑	0	1	RESET

(a) Positive-edge triggered

Inputs		Outputs		Comments
<i>D</i>	CLK	<i>Q</i>	$\bar{Q}$	
1	↓	1	0	SET
0	↓	0	1	RESET

(b) Negative-edge triggered

Floyd, Digital Fundamentals, 10<sup>th</sup> ed      © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**Flip-flops**

The J-K flip-flop is more versatile than the D flip flop. In addition to the clock input, it has two inputs, labeled *J* and *K*. When both *J* and *K* = 1, the output changes states (toggles) on the active clock edge (in this case, the rising edge).

Inputs			Outputs		Comments
<i>J</i>	<i>K</i>	CLK	<i>Q</i>	$\bar{Q}$	
0	0	↑	$Q_0$	$\bar{Q}_0$	No change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	$\bar{Q}_0$	$Q_0$	Toggle

Floyd, Digital Fundamentals, 10<sup>th</sup> ed      © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**Flip-flops**

**Example**

Determine the  $Q$  output for the  $J-K$  flip-flop, given the inputs shown.

Notice that the outputs change on the leading edge of the clock.

**Solution**

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**Flip-flops**

A D-flip-flop does not have a toggle mode like the J-K flip-flop, but you can hardwire a toggle mode by connecting  $\bar{Q}$  back to  $D$  as shown. This is useful in some counters as you will see in Chapter 8.

For example, if  $Q$  is LOW,  $\bar{Q}$  is HIGH and the flip-flop will toggle on the next clock edge. Because the flip-flop only changes on the active edge, the output will only change once for each clock pulse.

D flip-flop hardwired for a toggle mode

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**Flip-flops**

Synchronous inputs are transferred in the triggering edge of the clock (for example the  $D$  or  $J-K$  inputs). Most flip-flops have other inputs that are *asynchronous*, meaning they affect the output independent of the clock.

Two such inputs are normally labeled preset ( $PRE$ ) and clear ( $CLR$ ). These inputs are usually active LOW. A J-K flip flop with active LOW preset and CLR is shown.

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**Flip-flops**

**Example**  
Determine the  $Q$  output for the  $J-K$  flip-flop, given the inputs shown.

**Solution**

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**Flip-flop Characteristics**

**Propagation delay time** is specified for the rising and falling outputs. It is measured between the 50% level of the clock to the 50% level of the output transition.

The typical propagation delay time for the 74AHC family (CMOS) is 4 ns. Even faster logic is available for specialized applications.

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**Flip-flop Characteristics**

Another **propagation delay time** specification is the time required for an *asynchronous* input to cause a change in the output. Again it is measured from the 50% levels. The 74AHC family has specified delay times under 5 ns.

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**Flip-flop Characteristics**

**Set-up time and hold time** are times required before and after the clock transition that data must be present to be reliably clocked into the flip-flop.

**Setup time** is the minimum time for the data to be present before the clock.

**Hold time** is the minimum time for the data to remain after the clock.

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**Flip-flop Characteristics**

Other specifications include maximum clock frequency, minimum pulse widths for various inputs, and power dissipation. The power dissipation is the product of the supply voltage and the average current required.

A useful comparison between logic families is the **speed-power product** which uses two of the specifications discussed: the average propagation delay and the average power dissipation. The unit is energy.

**Example** What is the speed-power product for 74AHC74A? Use the data from Table 7-5 to determine the answer.

**Solution** From Table 7-5, the average propagation delay is 4.6 ns. The quiescent power dissipated is 1.1 mW. Therefore, the speed-power product is **5 pJ**

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**Flip-flop Applications**

Principal flip-flop applications are for temporary data storage, as frequency dividers, and in counters (which are covered in detail in Chapter 8).

Typically, for **data storage** applications, a group of flip-flops are connected to parallel data lines and clocked together. Data is stored until the next clock pulse.

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**Flip-flop Applications**

For **frequency division**, it is simple to use a flip-flop in the toggle mode or to chain a series of toggle flip flops to continue to divide by two.

One flip-flop will divide  $f_{in}$  by 2, two flip-flops will divide  $f_{in}$  by 4 (and so on). A side benefit of frequency division is that the output has an exact 50% duty cycle.

Waveforms:

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**One-Shots**

The **one-shot** or **monostable** multivibrator is a device with only one stable state. When triggered, it goes to its unstable state for a predetermined length of time, then returns to its stable state.

For most one-shots, the length of time in the unstable state ( $t_w$ ) is determined by an external RC circuit.

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**One-Shots**

Nonretriggerable one-shots do not respond to any triggers that occur during the unstable state.

Retriggerable one-shots respond to any trigger, even if it occurs in the unstable state. If it occurs during the unstable state, the state is extended by an amount equal to the pulse width.

Retriggerable one-shot:

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

---



**Summary**

**One-Shots**

An application for a retriggerable one-shot is a power failure detection circuit. Triggers are derived from the ac power source, and continue to retrigger the one shot. In the event of a power failure, the one-shot is not triggered and an alarm can be initiated.

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**The 555 timer**

The 555 timer can be configured in various ways, including as a one-shot. A basic one shot is shown. The pulse width is determined by  $R_1C_1$  and is approximately  $t_w = 1.1R_1C_1$ .

The trigger is a negative-going pulse.

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**The 555 timer**

**Example** Determine the pulse width for the circuit shown.

**Solution**  $t_w = 1.1R_1C_1 = 1.1(10\text{ k}\Omega)(2.2\text{ }\mu\text{F}) = 24.2\text{ ms}$

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

---

**Summary**

**The 555 timer**

The 555 can be configured as a basic astable multivibrator with the circuit shown. In this circuit  $C_1$  charges through  $R_1$  and  $R_2$  and discharges through only  $R_2$ . The output frequency is given by:

$$f = \frac{1.44}{(R_1 + 2R_2)C_1}$$

The frequency and duty cycle are set by these components.

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

**Summary**

**The 555 timer**

Given the components, you can read the frequency from the chart. Alternatively, you can use the chart to pick components for a desired frequency.

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

**Selected Key Terms**

**Latch** A bistable digital circuit used for storing a bit.

**Bistable** Having two stable states. Latches and flip-flops are bistable multivibrators.

**Clock** A triggering input of a flip-flop.

**D flip-flop** A type of bistable multivibrator in which the output assumes the state of the *D* input on the triggering edge of a clock pulse.

**J-K flip-flop** A type of flip-flop that can operate in the SET, RESET, no-change, and toggle modes.

Floyd, Digital Fundamentals, 10<sup>th</sup> ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

---

---

### Selected Key Terms

**Propagation delay time** The interval of time required after an input signal has been applied for the resulting output signal to change.

**Set-up time** The time interval required for the input levels to be on a digital circuit.

**Hold time** The time interval required for the input levels to remain steady to a flip-flop after the triggering edge in order to reliably activate the device.

**Timer** A circuit that can be used as a one-shot or as an oscillator.

Floyd, Digital Fundamentals, 10<sup>th</sup> ed      © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---

## Quiz

1. The output of a D latch will not change if

- the output is LOW
- Enable is not active
- D is LOW
- all of the above

© 2008 Pearson Education

---

---

---

---

---

---

---

---

## Quiz

2. The D flip-flop shown will

- set on the next clock pulse
- reset on the next clock pulse
- latch on the next clock pulse
- toggle on the next clock pulse

© 2008 Pearson Education

---

---

---

---

---

---


---

---

### Quiz

3. For the J-K flip-flop shown, the number of inputs that are asynchronous is

- a. 1
- b. 2
- c. 3
- d. 4

 

© 2008 Pearson Education

---

---

---

---

---

---


---

---

### Quiz

4. Assume the output is initially HIGH on a leading edge triggered J-K flip flop. For the inputs shown, the output will go from HIGH to LOW on which clock pulse?

- a. 1
- b. 2
- c. 3
- d. 4

 

© 2008 Pearson Education

---

---

---

---

---

---


---

---

### Quiz

5. The time interval illustrated is called

 - a.  $t_{PHL}$
- b.  $t_{PLH}$
- c. set-up time
- d. hold time



© 2008 Pearson Education

---

---

---

---

---

---


---

---

### Quiz

6. The time interval illustrated is called

 - a.  $t_{PHL}$
- b.  $t_{PLH}$
- c. set-up time
- d. hold time



© 2008 Pearson Education

---

---

---

---

---

---


---

---

### Quiz

7. The application illustrated is a

 - a. astable multivibrator
- b. data storage device
- c. frequency multiplier
- d. frequency divider



© 2008 Pearson Education

---

---

---

---

---

---


---

---

### Quiz

8. The application illustrated is a

 - a. astable multivibrator
- b. data storage device
- c. frequency multiplier
- d. frequency divider



© 2008 Pearson Education

---

---

---

---

---

---

---

---

## Quiz

9. A retriggerable one-shot with an active HIGH output has a pulse width of 20 ms and is triggered from a 60 Hz line. The output will be a

- a. series of 16.7 ms pulses
- b. series of 20 ms pulses
- c. constant LOW
- d. constant HIGH

© 2008 Pearson Education

---

---

---

---

---

---


---

---

## Quiz

10. The circuit illustrated is a

 - a. astable multivibrator
- b. monostable multivibrator
- c. frequency multiplier
- d. frequency divider



© 2008 Pearson Education

---

---

---

---

---

---

---

---

## Quiz

Answers:

- |      |       |
|------|-------|
| 1. b | 6. d  |
| 2. d | 7. d  |
| 3. b | 8. b  |
| 4. c | 9. d  |
| 5. b | 10. a |

Floyd, Digital Fundamentals, 10<sup>th</sup> ed

© 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

---

---

---

---

---

---

---

---