

# Switches and Relays

Daniel Kohn  
University of Memphis  
Department of Engineering Technology  
TECH 3821 – Industrial Electronics  
Fall 2023

1

---

---

---

---

---


---

---


---

### Switches


- Definition - a device for making and breaking the connection in an electric circuit.
- Types (Action):




Toggle




Rocker




Pushbutton



Limit



Rotary



Slide

2

---

---

---

---

---


---

---


---

### Switches (Cont)


- Types (Electronic Connections):




A Normal Open contact (NO)




A Normal Closed contact (NC)



spst      dpst



spdt      dpdt

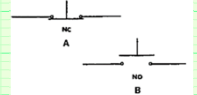

NC  
A

NO  
B

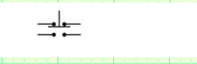


FIGURE 11-11. Push Buttons.

3

---

---

---

---

---

---

---

---

**Switches (Cont)**


What does SPST, SPDT, DPST, and DPDT mean?

SP and DP refer to single pole and double pole; ST and DT refer to single throw and double throw.

Pole refers to the number of circuits controlled by the switch: SP switches control only one electrical circuit. DP switches control two independent circuits (and act like two identical switches that are mechanically linked). Do not confuse 'pole' with 'terminal'. The DPST switch, for example, has four terminals, but it is a DP, not a 4P switch.

Throw refers to the extreme position of the actuator. ST switches close a circuit at only one position. The other position of the handle is Off. DT switches close a circuit in the Up position, as well as the Down position (On-Off). A DT switch can also have a center position (frequently On-Off-On).

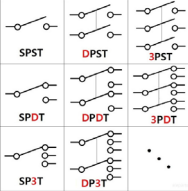Single pole/throw and double pole/throw switches are by far the most common switches, but triple and quadruple configurations are also available. They are commonly denoted 3PST, 3PDT, 4PDT, etc.



<https://www.instructables.com/printing-3d-4p-st-4p-dt-4p-dt/>

4

---

---

---

---

---

---

---

---

---


---

---

---

**Switches**

- SPDT

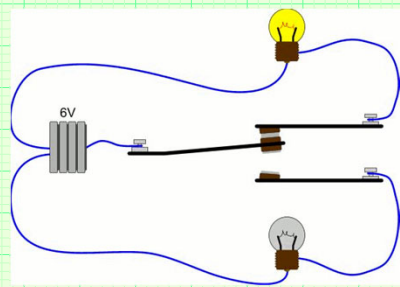

<https://www.instructables.com/3d-printing-a-3-position-switch/>

5

---

---

---

---

---

---

---

---

---

---

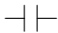

---

---

**Switches**

- How is NORMAL determined?
  - The normal state of a switch is that where it is unactuated. For process switches, this is the condition its in when sitting on a shelf, uninstalled.
  - A switch that is open when unactuated is called normally-open. A switch that is closed when unactuated is called normally-closed. Sometimes the terms "normally-open" and "normally-closed" are abbreviated N.O. and N.C., respectively.

Generic switch contact designation

<i>Normally-open</i>	<i>Normally-closed</i>
	

6

---

---

---

---

---

---

---

---

---

---

---

---

○

## Switch Types (cont)

[http://www.musicfromouterspace.com/analogsynth\\_new/ELECTRONICS/sw/switches.html](http://www.musicfromouterspace.com/analogsynth_new/ELECTRONICS/sw/switches.html)

○

7

---

---

---

---

---


---

---

---

Relay

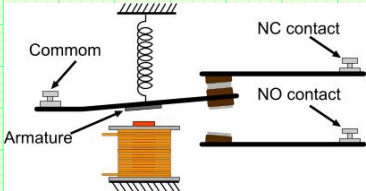- A Relay is an Electromechanical device that uses an electromagnet to change the status of a switch contact.



[http://pocheraven.com/wikipedia/how\\_Relays\\_Work/](http://pocheraven.com/wikipedia/how_Relays_Work/)

○

8

---

---

---

---

---


---

---

---

Relay

- Example

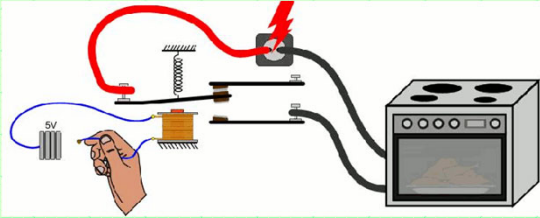

○

9

---

---

---


---

---

---

---

---

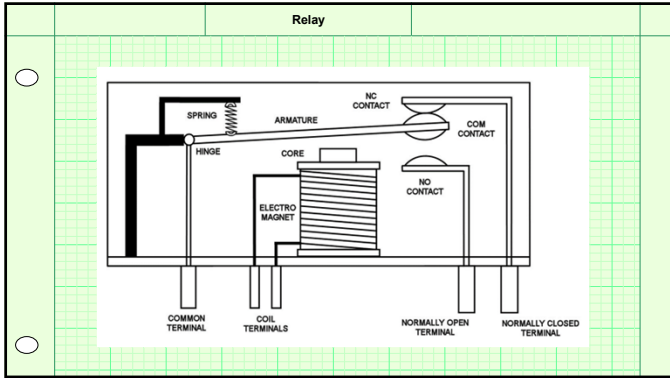

10

---

---

---


---

---

---

---

---

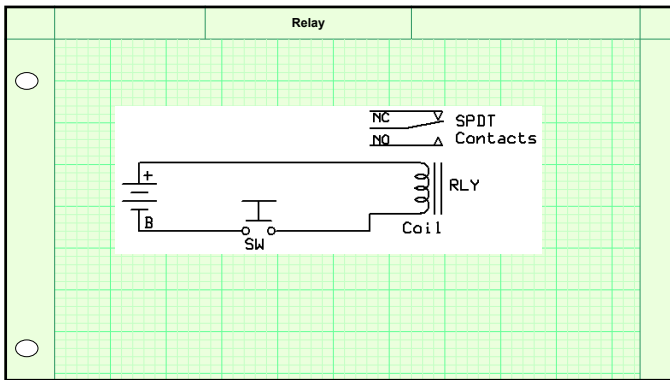

11

---

---

---


---

---

---

---

---

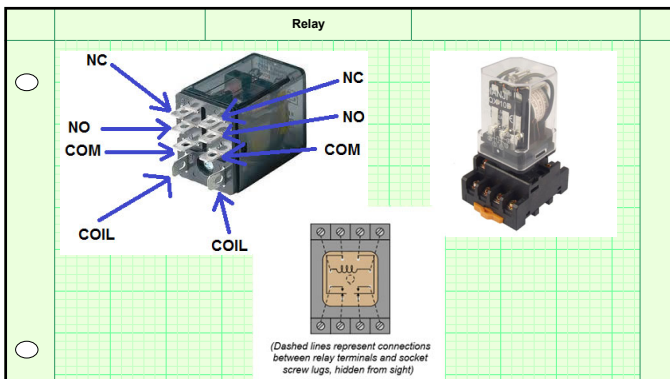

12

---

---

---

---

---

---

---

---



13

---

---

---


---

---

---

---

---

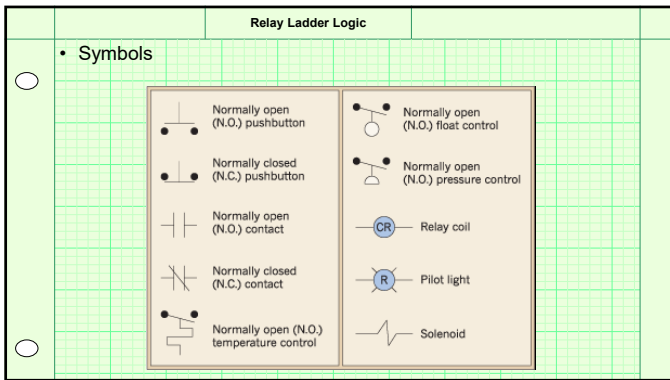

14

---

---

---


---

---

---

---

---

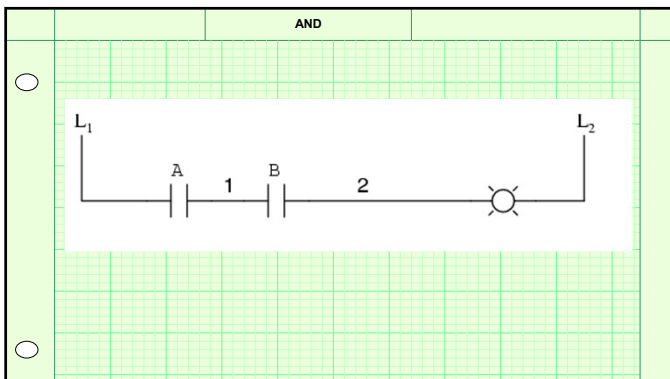

15

---

---

---


---

---

---

---

---

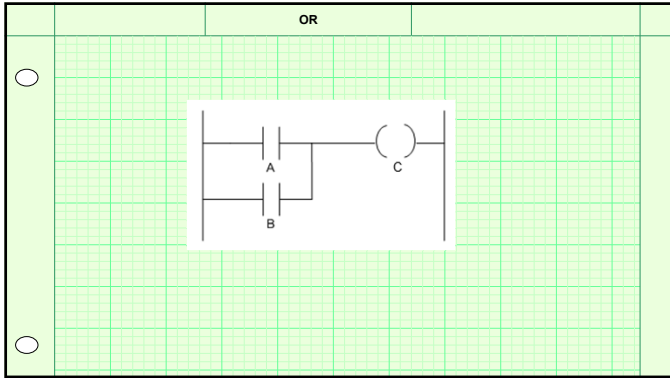

16

---

---

---


---

---

---

---

---

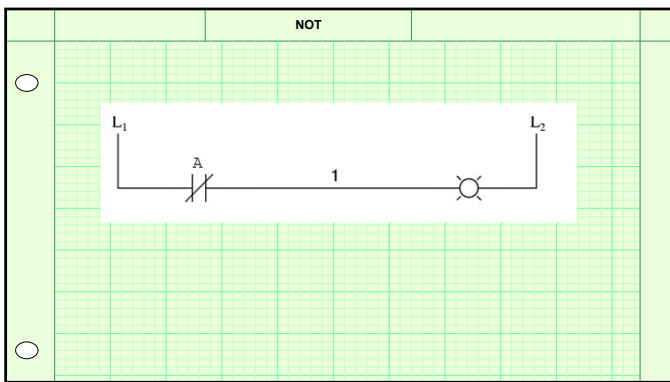

17

---

---

---


---

---

---

---

---

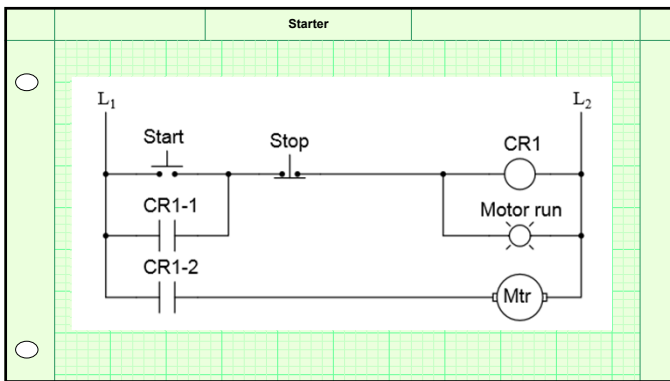

18

---

---

---


---

---

---

---

---

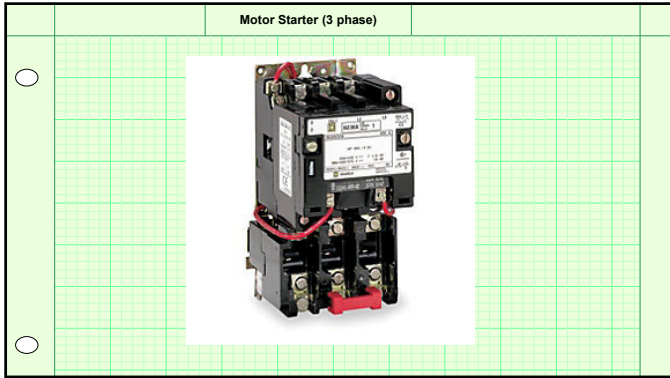

19

---

---


---

---

---

---

---

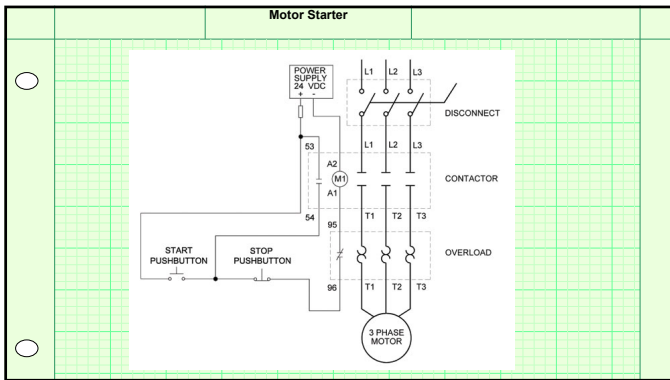

20

---

---

---

---

---

---

---