

Analog to Digital Converters

By: Byron Johns, Danny Carpenter Stephanie Pohl,
Harry "Bo" Marr

http://ume.gatech.edu/mechatronics_course/FADC_F05.ppt

(unless otherwise marked)



1

Presentation Outline

- Introduction: Analog vs. Digital?
- Examples of ADC Applications
- Types of A/D Converters
- Successive Approximation ADC



2

Analog Signals

Analog signals – directly measurable quantities
in terms of some other quantity

Examples:

- Thermometer – mercury height rises as temperature rises
- Car Speedometer – Needle moves farther right as you accelerate
- Stereo – Volume increases as you turn the knob.



3


Digital Signals

Digital Signals – have only two states. For digital computers, we refer to binary states, 0 and 1. “1” can be on, “0” can be off.

Examples:

- Light switch can be either on or off
- Door to a room is either open or closed

4

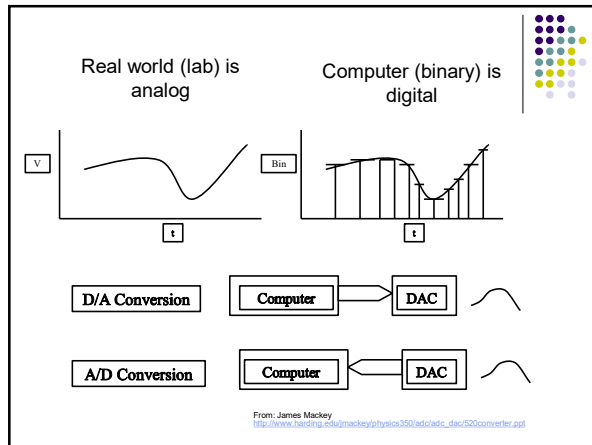

5

Examples of A/D Applications


- Microphones – take your voice varying pressure waves in the air and convert them into varying electrical signals
- Strain Gages – determines the amount of strain (change in dimensions) when a stress is applied
- Thermocouple – temperature measuring device converts thermal energy to electric energy
- Voltmeters
- Digital Multimeters

6

Just what does an A/D converter DO?



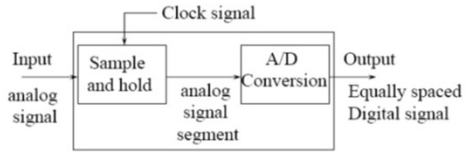- Converts analog signals into binary words



7

Analog → Digital Conversion 2-Step Process:



- Quantizing - breaking down analog value is a set of finite states
- Encoding - assigning a digital word or number to each state and matching it to the input signal

8

Step 1: Quantizing



Example:

You have 0-10V signals. Separate them into a set of discrete states with 1.25V increments. (How did we get 1.25V? See next slide...)

Output States	Discrete Voltage Ranges (V)
0	0.00-1.25
1	1.25-2.50
2	2.50-3.75
3	3.75-5.00
4	5.00-6.25
5	6.25-7.50
6	7.50-8.75
7	8.75-10.0

9

Quantizing



The number of possible states that the converter can output is:

$$N=2^n$$

where n is the number of bits in the AD converter

Example: For a 3 bit A/D converter, $N=2^3=8$.

Analog quantization size:

$$Q=(V_{\max}-V_{\min})/N = (10V - 0V)/8 = 1.25V$$

10

Encoding



- Here we assign the digital value (binary number) to each state for the computer to read.

Output States	Output Binary Equivalent
0	000
1	001
2	010
3	011
4	100
5	101
6	110
7	111

11

Accuracy of A/D Conversion



There are two ways to best improve accuracy of A/D conversion:

- increasing the resolution which improves the accuracy in measuring the amplitude of the analog signal.
- increasing the sampling rate which increases the maximum frequency that can be measured.

12


Resolution



- Resolution (number of discrete values the converter can produce) = Analog Quantization size (Q)
($Q = V_{\text{range}} / 2^n$, where V_{range} is the range of analog voltages which can be represented)
- limited by signal-to-noise ratio (should be around 6dB)
- In our previous example: $Q = 1.25V$, this is a high resolution. A lower resolution would be if we used a 2-bit converter, then the resolution would be $10/2^2 = 2.50V$.

13

Sampling Rate

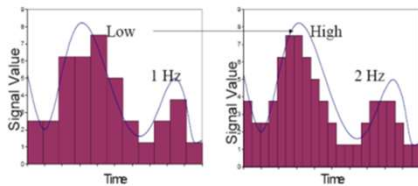

Frequency at which ADC evaluates analog signal. As we see in the second picture, evaluating the signal more often more accurately depicts the ADC signal.

14

Aliasing



- Occurs when the input signal is changing much faster than the sample rate.

For example, a 2 kHz sine wave being sampled at 1.5 kHz would be reconstructed as a 500 Hz (the aliased signal) sine wave.

Nyquist Rule:


- Use a sampling frequency at least twice as high as the maximum frequency in the signal to avoid aliasing.

15

Overall Better Accuracy



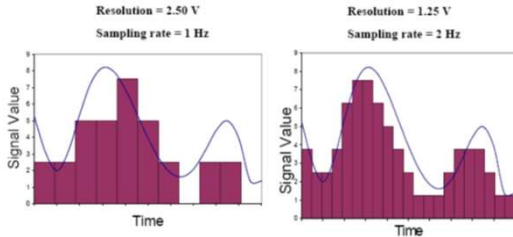- Increasing both the sampling rate and the resolution you can obtain better accuracy in your AD signals.



16

A/D Converter Types By Danny



Carpenter

- Converters
 - Flash ADC
 - Dual Slope (integrating) ADC
 - Successive Approximation ADC

17


Flash ADC



- Consists of a series of comparators, each one comparing the input signal to a unique reference voltage.
- The comparator outputs connect to the inputs of a priority encoder circuit, which produces a binary output

18

Flash ADC Circuit

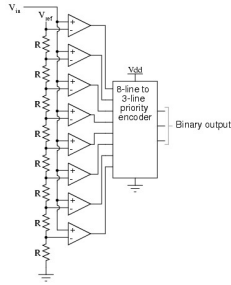


19

How Flash Works

- As the analog input voltage exceeds the reference voltage at each comparator, the comparator outputs will sequentially saturate to a high state.
- The priority encoder generates a binary number based on the highest-order active input, ignoring all other active inputs.

20

ADC Output

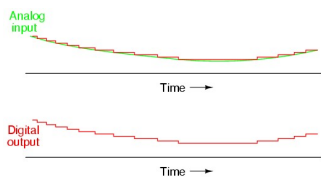

21

Flash



Advantages


- Simplest in terms of operational theory
- Most efficient in terms of speed, very fast
 - limited only in terms of comparator and gate propagation delays

Disadvantages

- Lower resolution
- Expensive
- For each additional output bit, the number of comparators is doubled
 - i.e. for 8 bits, 256 comparators needed

22

Dual Slope Converter

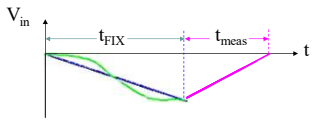

- The sampled signal charges a capacitor for a fixed amount of time
- By integrating over time, noise integrates out of the conversion
- Then the ADC discharges the capacitor at a fixed rate with the counter counts the ADC's output bits. A longer discharge time results in a higher count

23

Dual Slope Converter



Advantages

- Input signal is averaged
- Greater noise immunity than other ADC types
- High accuracy

Disadvantages

- Slow
- High precision external components required to achieve accuracy

24

Digital-to-Analog Conversion [DAC]

http://www-personal.engin.umich.edu/~jwvm/ece414/PowerPoint/8_A-D_converter.ppt



25

Digital-to-Analog Conversion



- When data is in binary form, the 0's and 1's may be of several forms such as the TTL form where the logic zero may be a value up to 0.8 volts and the 1 may be a voltage from 2 to 5 volts.
- The data can be converted to clean digital form using gates which are designed to be on or off depending on the value of the incoming signal.

26


Digital-to-Analog Conversion



- Data in clean binary digital form can be converted to an analog form by using a summing amplifier.
- For example, a simple 4-bit D/A converter can be made with a four-input summing amplifier.


27

R-2R Ladder DAC

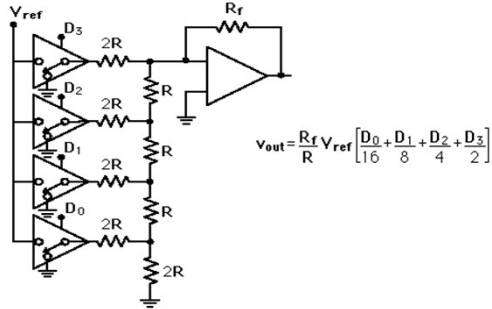

28

R-2R Ladder DAC

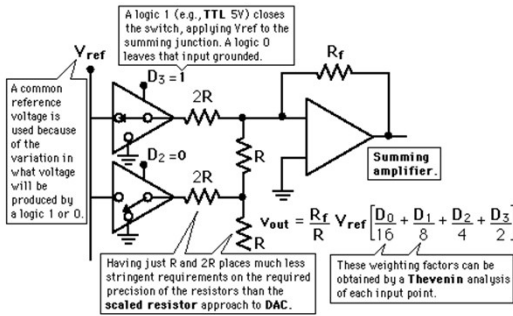


29

R-2R Ladder DAC

- The summing amplifier with the R-2R ladder of resistances shown produces the output where the D's take the value 0 or 1.
- The digital inputs could be TTL voltages which close the switches on a logical 1 and leave it grounded for a logical 0.
- This is illustrated for 4 bits, but can be extended to any number with just the resistance values R and 2R.

30

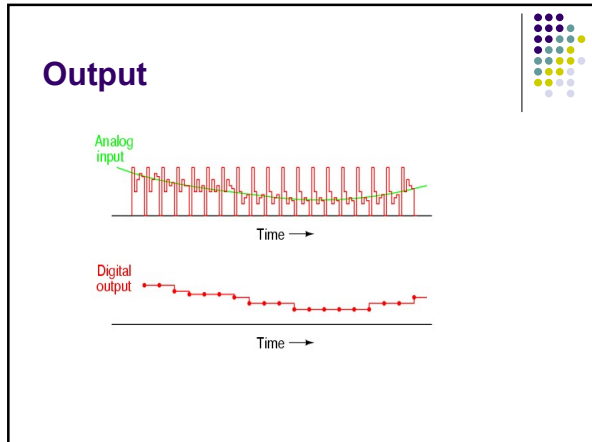

34

Successive Approximation

Advantages

- Capable of high speed and reliable
- Medium accuracy compared to other ADC types
- Good tradeoff between speed and cost
- Capable of outputting the binary number in serial (one bit at a time) format.

Disadvantages

- Higher resolution successive approximation ADC's will be slower
- Speed limited to ~5Msps

35

ADC Types Comparison

The bar chart shows the resolution range in bits for four ADC types. The x-axis is labeled 'Resolution (Bits)' and ranges from 0 to 25. The y-axis lists the ADC types: Dual Slope, Flash, Successive Approx, and Sigma-Delta.

Type	Speed (relative)	Cost (relative)
Dual Slope	Slow	Med
Flash	Very Fast	High
Successive Appox	Medium – Fast	Low
Sigma-Delta	Slow	Low

36

Successive Approximation Example



- Spreadsheet examples

37

Successive Approximation Example



- 10 bit resolution or 0.0009765625V of Vref
- $V_{in} = .6$ volts
- $V_{ref} = 1$ volts
- Find the digital value of V_{in}

Bit	Voltage
9	.5
8	.25
7	.125
6	.0625
5	.03125
4	.015625
3	.0078125
2	.00390625
1	.001952125
0	.0009765625

38

Successive Approximation



- MSB (bit 9)
 - Divided V_{ref} by 2
 - Compare $V_{ref}/2$ with V_{in}
 - If V_{in} is greater than $V_{ref}/2$, turn MSB on (1)
 - If V_{in} is less than $V_{ref}/2$, turn MSB off (0)
 - $V_{in} = 0.6V$ and $V = 0.5$
 - Since $V_{in} > V$, MSB = 1 (on)

1									
---	--	--	--	--	--	--	--	--	--

39

Successive Approximation



- Next Calculate MSB-1 (bit 8)
 - Compare $V_{in}=0.6\text{ V}$ to $V=V_{ref}/2 + V_{ref}/4= 0.5+0.25=0.75\text{V}$
 - Since $0.6<0.75$, MSB is turned off
- Calculate MSB-2 (bit 7)
 - Go back to the last voltage that caused it to be turned on (Bit 9) and add it to $V_{ref}/8$, and compare with V_{in}
 - Compare V_{in} with $(0.5+V_{ref}/8)=0.625$
 - Since $0.6<0.625$, MSB is turned off

1	0	0							
---	---	---	--	--	--	--	--	--	--

40

Successive Approximation



- Calculate the state of MSB-3 (bit 6)
 - Go to the last bit that caused it to be turned on (In this case MSB-1) and add it to $V_{ref}/16$, and compare it to V_{in}
 - Compare V_{in} to $V= 0.5 + V_{ref}/16= 0.5625$
 - Since $0.6>0.5625$, MSB-3=1 (turned on)

MSB	MSB-1	MSB-2	MSB-3	...					
1	0	0	1						

41

Successive Approximation




- This process continues for all the remaining bits.

•Digital Results:

MSB	MSB-1	MSB-2	MSB-3	...					LSB
1	0	0	1	1	0	0	1	1	0

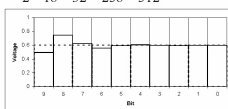•Results: $\frac{1}{2} + \frac{1}{16} + \frac{1}{32} + \frac{1}{256} + \frac{1}{512} = .599609375\text{ V}$



42
