


2

Master vs. Slave

- Master begins the communication by pulling down the CE pin of slave.
- Master makes the clock for communication

SPI internal circuit

 - A shift register in the master and another in the slave
- By each clock, a bit is shifted out from the master's shift register into the slave shift register and a bit is shifted from slave to master.



4

