



1

Summary

Binary Addition

The rules for binary addition are

$0 + 0 = 0$	Sum = 0, carry = 0
$0 + 1 = 0$	Sum = 1, carry = 0
$1 + 0 = 0$	Sum = 1, carry = 0
$1 + 1 = 10$	Sum = 0, carry = 1

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

2

Summary

Half-Adder

Basic rules of binary addition are performed by a **half adder**, which has two binary inputs (*A* and *B*) and two binary outputs (Carry out and Sum).

The inputs and outputs can be summarized on a truth table.

Inputs		Outputs	
<i>A</i>	<i>B</i>	<i>C_{out}</i>	Σ
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

The logic symbol and equivalent circuit are:

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

3

Summary

Binary Addition

When an input carry = 1 due to a previous result, the rules are

$1 + 0 + 0 = 01$	Sum = 1, carry = 0
$1 + 0 + 1 = 10$	Sum = 0, carry = 1
$1 + 1 + 0 = 10$	Sum = 0, carry = 1
$1 + 1 + 1 = 10$	Sum = 1, carry = 1

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

4

Summary

Full-Adder

By contrast, a **full adder** has three binary inputs (*A*, *B*, and Carry in) and two binary outputs (Carry out and Sum). The truth table summarizes the operation.

A full-adder can be constructed from two half adders as shown:

Inputs			Outputs	
A	B	C _{in}	C _{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

5

Summary

Full-Adder

Example

For the given inputs, determine the intermediate and final outputs of the full adder.

Solution The first half-adder has inputs of 1 and 0; therefore the Sum = 1 and the Carry out = 0.

The second half-adder has inputs of 1 and 1; therefore the Sum = 0 and the Carry out = 1.

The OR gate has inputs of 1 and 0, therefore the final carry out = 1.

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

6

Summary

Full-Adder

Notice that the result from the previous example can be read directly on the truth table for a full adder.

Inputs			Outputs	
A	B	C _{in}	C _{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

7

Summary

Binary Addition

Example Add the binary numbers 00111 and 10101 and show the equivalent decimal addition.

Solution

0 1 1 1	7
00111	7
10101	21
11100	= 28

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

8

Summary

Parallel Adders

Full adders are combined into parallel adders that can add binary numbers with multiple bits. A 4-bit adder is shown.

The output carry (C_4) is not ready until it propagates through all of the full adders. This is called *ripple carry*, delaying the addition process.

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

9

Summary

1's Complement

The 1's complement of a binary number is just the inverse of the digits. To form the 1's complement, change all 0's to 1's and all 1's to 0's.

For example, the 1's complement of **11001010** is **00110101**

In digital circuits, the 1's complement is formed by using inverters:

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

13

Summary

2's Complement

The 2's complement of a binary number is found by adding 1 to the LSB of the 1's complement.

Recall that the 1's complement of **11001010** is **00110101** (1's complement)

To form the 2's complement, add 1:

$$\begin{array}{r} 00110101 \text{ (1's complement)} \\ +1 \\ \hline 00110110 \text{ (2's complement)} \end{array}$$

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

14

Summary

Signed Binary Numbers

There are several ways to represent signed binary numbers. In all cases, the MSB in a signed number is the sign bit, that tells you if the number is positive or negative.

Computers use a modified 2's complement for signed numbers. Positive numbers are stored in *true form* (with a 0 for the sign bit) and negative numbers are stored in *complement form* (with a 1 for the sign bit).

For example, the positive number 58 is written using 8-bits as **00111010** (true form).

Sign bit Magnitude bits

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

15

Summary

Signed Binary Numbers

Negative numbers are written as the 2's complement of the corresponding positive number.

The negative number -58 is written as:
 $-58 = 11000110$ (complement form)

↑ Sign bit ↓ Magnitude bits

An easy way to read a signed number that uses this notation is to assign the sign bit a column weight of -128 (for an 8-bit number). Then add the column weights for the 1's.

Example Assuming that the sign bit = -128, show that 11000110 = -58 as a 2's complement signed number:

Solution Column weights: $-128 \ 64 \ 32 \ 16 \ 8 \ 4 \ 2 \ 1.$

1	1	0	0	0	1	1	0	
-128	$+64$				$+4$	$+2$		$= -58$

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

16

Circuit for 2's complement Numbers

Fig. 3-31 Adder-Subtractor Circuit

- **No Correction is needed** if the signed numbers are in 2's complement representation

Floyd, Digital Fundamentals, 10th ed © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

17
