



# Operational Amplifiers

From:  
[http://ume.gatech.edu/mechatronics\\_course/OpAmp\\_F11.ppt](http://ume.gatech.edu/mechatronics_course/OpAmp_F11.ppt)



1

---

---

---


---

---

---


---

---



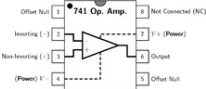
## What is an Op-Amp? – The Surface


- An Operational Amplifier (Op-Amp) is an integrated circuit that uses external voltage to amplify the input through a very high gain.
- We recognize an Op-Amp as a mass-produced component found in countless electronics.



What an Op-Amp looks like to a lay-person



What an Op-Amp looks like to an engineer



2

---

---

---


---

---

---


---


---


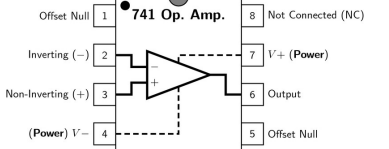
## What is an Op-Amp? – The Layout

- There are 8 pins in a common Op-Amp, like the 741 which is used in many instructional courses.





3

---

---

---

---

---

---

---

---

## What is an Op-Amp? – The Inside

- The actual count varies, but an Op-Amp contains several Transistors, Resistors, and a few Capacitors and Diodes.
- For simplicity, an Op-Amp is often depicted as this:

Georgia Tech

4

---

---

---

---

---

---

---

---

## History of the Op-Amp – The Dawn

- Before the Op-Amp: Harold S. Black develops the feedback amplifier for the Western Electric Company (1920-1930)

Georgia Tech

5

---

---

---

---

---

---

---

---

## History of the Op-Amp – The Dawn

- **The Vacuum Tube Age**
- The First Op-Amp: (1930 – 1940) Designed by Karl Swartzel for the Bell Labs M9 gun director
- Uses 3 vacuum tubes, only one input, and  $\pm 350$  V to attain a gain of 90 dB
- Loebe Julie then develops an Op-Amp with two inputs: Inverting and Non-inverting

Georgia Tech

6

---

---

---


---

---

---

---


---



### History of the Op-Amp – The Shift

- The end of Vacuum Tubes was built up during the 1950's-1960's to the advent of solid-state electronics

1. The Transistor
2. The Integrated Circuit
3. The Planar Process



7

---

---

---


---

---

---




---

---



### History of the Op-Amp – The Shift

- 1960s: beginning of the Solid State Op-Amp
- Example: GAP/R P45 (1961 – 1971)
  - Runs on  $\pm 15$  V, but costs \$118 for 1 – 4
- The GAP/R PP65 (1962) makes the Op-Amp into a circuit component as a potted module

8

---

---

---


---

---

---


---

---



### History of the Op-Amp – The Evolution

- The solid-state decade saw a proliferation of Op-Amps
  - Model 121, High Speed FET family, etc.
- Robert J. Widlar develops the  $\mu$ A702 Monolithic IC Op-Amp (1963) and shortly after the  $\mu$ A709
- Fairchild Semiconductor vs. National Semiconductor
  - National: The LM101 (1967) and then the LM101A (1968) (both by Widlar)
  - Fairchild: The "famous"  $\mu$ A741 (by Dave Fullager 1968) and then the  $\mu$ A748 (1969)



9

---

---

---

---

---

---

---


---

## Mathematics of the Op-Amp

- The gain of the Op-Amp itself is calculated as:  

$$G = V_{out} / (V_+ - V_-)$$
- The maximum output is the power supply voltage
- When used in a circuit, the gain of the circuit (as opposed to the op-amp component) is:  

$$A_v = V_{out} / V_{in}$$



10

---

---

---

---

---

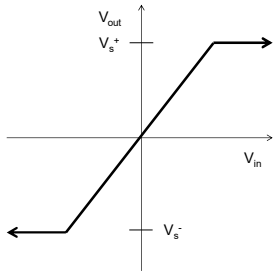

---

---

---

## Op-Amp Saturation

- As mentioned earlier, the maximum output value is the **supply voltage**, positive and negative.
- The gain (G) is the slope between saturation points.

11

---

---

---

---

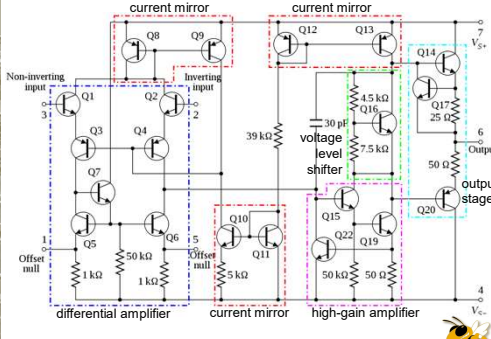

---

---

---

---

## 741 Op-Amp Schematic

12

---

---

---

---

---

---

---

---

### Op-Amp Characteristics

- Open-loop gain  $G$  is typically over 9000
  - But closed-loop gain is much smaller
- $R_{in}$  is very large (M $\Omega$  or larger)
- $R_{out}$  is small (75 $\Omega$  or smaller)
  - Effective output impedance in closed loop is very small

Georgia Tech

13

---

---

---

---

---

---

---

---

### Ideal Op-Amp Characteristics

- Open-loop gain  $G$  is infinite
- $R_{in}$  is infinite
  - Zero input current
- $R_{out}$  is zero

Georgia Tech

14

---

---

---

---

---

---

---

---

### Ideal Op-Amp Analysis

To analyze an op-amp feedback circuit:

- Assume no current flows into either input terminal
- Assume no current flows out of the output terminal
- Constrain:  $V_+ = V_-$

Georgia Tech

15

---

---

---

---

---

---

---

---

### Inverting Amplifier Analysis

$$V_{out} = -\frac{R_f}{R_{in}} V_{in}$$

16

---

---

---

---

---

---

---

---

### Non-Inverting Amplifier Analysis

$$V_{out} = V_{in} \left( 1 + \frac{R_2}{R_1} \right)$$

17

---

---

---

---

---

---

---

---

### Op-Amp Buffer

$V_{out} = V_{in}$   
 Isolates loading effects

18

---

---

---

---

---

---

---

---

### Op-Amp Differentiator

$$V_{out} = -RC \frac{dV_{in}}{dt}$$

19

---

---

---

---

---

---

---

---

### Op-Amp Integrator

$$V_{out} = - \int_0^t \frac{V_{in}}{RC} dt + V_{initial}$$

20

---

---

---

---

---

---

---

---

### Op-Amp Summing Amplifier

$$V_{out} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \right)$$

21

---

---

---

---

---

---



---

---

### Op-Amp Differential Amplifier

$$V_{out} = \frac{(R_f + R_1) R_g}{(R_g + R_2) R_1} V_2 - \frac{R_f}{R_1} V_1$$

If  $R_1 = R_2$  and  $R_f = R_g$ :  $V_{out} = \frac{R_f}{R_1} (V_2 - V_1)$

22

---

---

---

---

---

---

---

---

### Applications of Op-Amps

#### Filters

**Types:**



- Low pass filter
- High pass filter
- Band pass filter
- Cascading (2 or more filters connected together)

**Low pass filter**

Low pass filter transfer function →

$$H(s) = \frac{-R_2 \omega_c}{sR_1 + R_1 \omega_c}$$

Low pass filter Cutoff frequency →

$$\omega_c = \frac{1}{R_2 C}$$



23

---

---

---

---

---



---

---

---

### Applications of Op-Amps

- Electrocardiogram (EKG) Amplification
  - Need to measure difference in voltage from lead 1 and lead 2
  - 60 Hz interference from electrical equipment

24

---

---

---

---

---

---

---

---



## Applications of Op-Amps

- Simple EKG circuit
  - Uses differential amplifier to cancel common mode signal and amplify differential mode signal
- Realistic EKG circuit
  - Uses two non-inverting amplifiers to first amplify voltage from each lead, followed by differential amplifier
  - Forms an "instrumentation amplifier"

25

---

---

---

---

---

---

---

---

---

---

## Strain Gauge

Use a Wheatstone bridge to determine the strain of an element by measuring the change in resistance of a strain gauge

(No strain) Balanced Bridge  $R\#1 = R\#2$

(Strain) Unbalanced Bridge  $R\#1 \neq R\#2$

26

---

---

---

---

---

---

---

---

---

---

## Strain Gauge

### Half-Bridge Arrangement

Op amp used to amplify output from strain gauge

Using KCL at the inverting and non-inverting terminals of the op amp we find that  $\epsilon - V_o = 2\Delta R(R_t/R^2)$

27

---

---

---

---

---

---

---


---

---


---
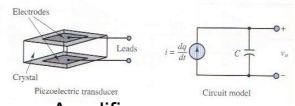
## Applications of Op-Amps

- Piezoelectric Transducer
  - Used to measure force, pressure, acceleration
  - Piezoelectric crystal generates an electric charge in response to deformation



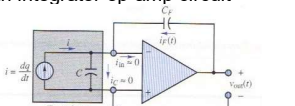- Use Charge Amplifier
  - Just an integrator op-amp circuit



Georgia Tech

28

---

---

---

---


---

---

---

---

## PID Controller – System Block Diagram

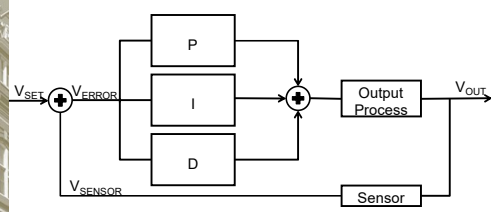

- Goal is to have  $V_{SET} = V_{OUT}$
- Remember that  $V_{ERROR} = V_{SET} - V_{SENSOR}$
- Output Process uses  $V_{ERROR}$  from the PID controller to adjust  $V_{out}$  such that it is  $\sim V_{SET}$

Georgia Tech

29

---

---

---

---

---


---

---

---

## Applications
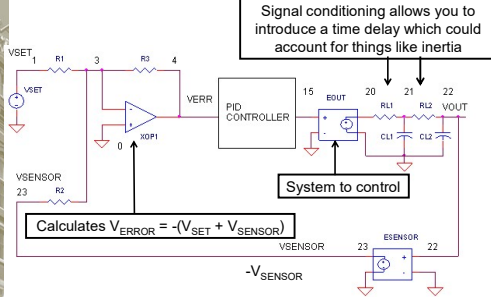
### PID Controller – System Circuit Diagram



Signal conditioning allows you to introduce a time delay which could account for things like inertia

Calculates  $V_{ERROR} = -(V_{SET} + V_{SENSOR})$

Source: [http://www.ecircuitcenter.com/Circuits/op\\_pid/op\\_pid.htm](http://www.ecircuitcenter.com/Circuits/op_pid/op_pid.htm)

Georgia Tech

30

---

---

---

---

---

---

---

---

### Applications

#### PID Controller – PID Controller Circuit Diagram

Adjust	Change
$K_p$	RP1, RP2
$K_i$	RI, CI
$K_d$	RD, CD

Georgia Tech

31

---

---

---

---

---

---

---

---

---

---

### Applications of Op-Amps

- Example of PI Control: Temperature Control

Thermal System we wish to automatically control the temperature of:

Block Diagram of Control System:

Georgia Tech

32

---

---

---

---

---

---

---

---

---

---

### Applications of Op-Amps

- Example of PI Control: Temperature Control

- Voltage Error Circuit:

- Proportional-Integral Control Circuit:

Georgia Tech

33

---

---

---

---

---


---

---

---


---

---



## References

- Cetinkunt, Sabri. Mechatronics. Hoboken, NJ: John Wiley & Sons Inc., 2007.
- Jung, Walter G. Op Amp Applications Handbook. Analog Devices, Inc., 2005.
- "Operational Amplifier."  
[http://en.wikipedia.org/wiki/Operational\\_amplifier](http://en.wikipedia.org/wiki/Operational_amplifier).
- "Operational Amplifier Applications."  
[http://en.wikipedia.org/wiki/Operational\\_amplifier\\_applications](http://en.wikipedia.org/wiki/Operational_amplifier_applications).



34

---

---

---


---

---

---


---

---



## References

- Rizzoni, G. *Principles and Applications of Electrical Engineering*, McGraw Hill, 2007.
- <http://web.njit.edu/~joelsd/electronics/Labs/ecqlab.pdf>



35

---

---

---


---

---

---


---

---



From: *Engineer's Mini-Notebook – Op Amp IC Circuits* by Forrest Mims III

## MORE OP AMP CIRCUITS



36

---

---

---

---

---

---

---

---

### Peak Detector

+V  
V = ±5 TO ±15 VOLTS

THIS OPAMP IS A VOLTAGE FOLLOWER THAT BUFFERS C1 FROM THE OUTPUT.

D1  
C1  
RESET 1 TO 10 μF

+V  
-V  
INPUT  
OUTPUT  
DRIFF  
TIME

37

---

---

---

---

---

---

---

---

### Clipper (non-inverting)

NON-INVERTING CLIPPER

+V  
V = ±5 TO ±15 V

INPUT  
OUTPUT  
R1  
R2  
D1  
D2

TYPICAL WAVEFORMS  
IN  
OUT  
GAIN = 1 + R2/R1  
VALUES SHOWN GIVE x1.1 GAIN.

38

---

---

---

---

---

---

---

---

### Comparators

NON-INVERTING COMPARATOR

INVERTING COMPARATOR

39

---

---

---

---

---

---

---

---

### Comparator (example)

Georgia Tech

40

---

---

---

---

---

---

---

---

### Window Comparator

Georgia Tech

41

---

---

---

---

---

---

---

---

### Bargraph

Georgia Tech

42

---

---

---

---

---

---

---

---

### Automatic Light

43

---

---

---

---

---

---

---

---

From: [https://en.wikipedia.org/wiki/Instrumentation\\_amplifier](https://en.wikipedia.org/wiki/Instrumentation_amplifier)

## INSTRUMENTATION AMPLIFIER

44

---

---

---

---

---

---

---

---

## Instrumentation Amp

- a type of differential amplifier
- input buffer amplifiers (no need to do impedance matching)
- Very low DC offset, low drift, low noise, very high open-loop gain, very high common-mode rejection ratio, and very high input impedances.

45

---

---

---


---

---

---


---

---



## Instrumentation Amp

- Great accuracy and stability of the circuit both short and long-term are required.
- instrumentation amplifier are shown schematically identical to a standard op-amp, but internally composed of 3 op-amps.



46

---

---

---


---

---


---

---


---



## Instrumentation Amp

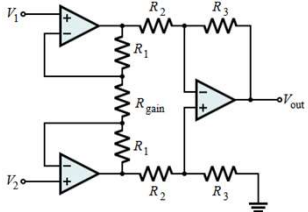

$$\frac{V_{out}}{V_2 - V_1} = \left( 1 + \frac{2R_1}{R_{gain}} \right) \frac{R_3}{R_2}$$



47

---

---

---

---

---

---

---

---